



INSTITUTO POLITÉCNICO NACIONAL



ESCUELA SUPERIOR DE CÓMPUTO

INGENIERIA EN SISTEMAS COMPUTACIONALES

MATERIA: DISEÑO DE SISTEMAS DIGITALES

PROFESOR: TESTA NAVA ALEXIS

PRESENTA:


RAMIREZ BENITEZ BRAYAN

GRUPO: 2CV18

ACTIVIDAD 4

CIUDAD DE MEXICO MARZO DE 2021

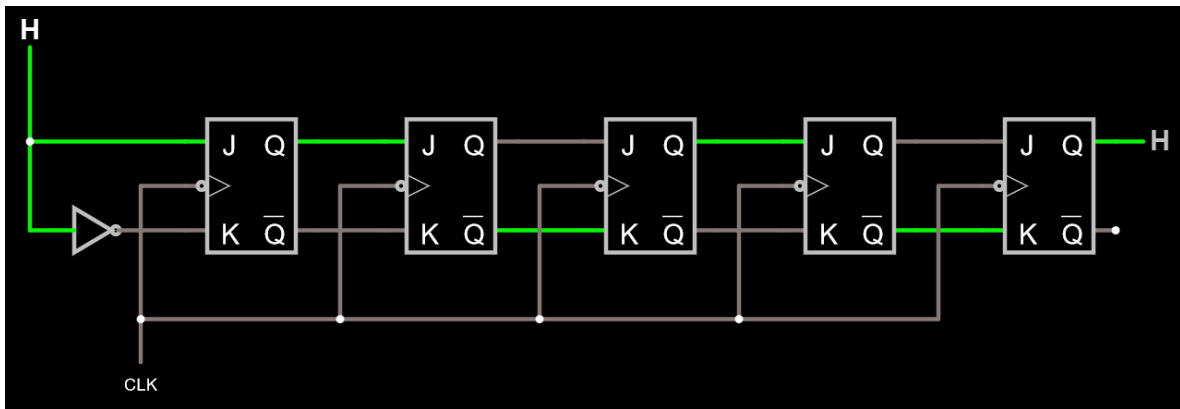Realizar en Falstad y HDL el diseño de los registros:
Entrada Serie - salida Serie (Con JK)



Enlace: <https://tinyurl.com/yhrdpeji>

```

P42 [Device - PALCE22V10-25PC/PI] - Galaxy - [P42.vhd]
File Edit View Format Project Compile Templates Bookmarks Tools Window Help

Source Files - Project: P42
├── PD.vhd
├── P42.vhd
└── Rom Files

1 LIBRARY IEEE;
2 USE IEEE.STD_LOGIC_1164.ALL;
3
4 ENTITY SP IS
5     PORT (clk, J, K, clear : in std_logic;
6           Q : OUT STD_LOGIC);
7 END SP;
8
9 ARCHITECTURE BEHAV OF SP IS
10
11     SIGNAL JK, JK0, JK1, JK2, JK3: STD_LOGIC_VECTOR (1 downto 0);
12     SIGNAL Q0, Q1, Q2, Q3, Q4 : STD_LOGIC;
13
14 BEGIN
15     JK <= J&K;
16     JK0 <= Q0&(NOT Q0);
17     JK1 <= Q1&(NOT Q1);
18     JK2 <= Q2&(NOT Q2);
19     JK3 <= Q3&(NOT Q3);
20
21     PROCESS (clear, clk)
22     BEGIN
23         IF (clear = '1') THEN
24             Q1 <= '0';
25         ELSIF ((clk'EVENT) AND (clk = '1')) THEN
26             CASE JK IS
27                 WHEN "00" => Q0 <= Q0;
28                 WHEN "01" => Q0 <= '0';
29                 WHEN "10" => Q0 <= '1';
30                 WHEN OTHERS => Q0 <= NOT Q0;
31             END CASE;
32
33             CASE JK0 IS
34                 WHEN "00" => Q1 <= Q1;
35                 WHEN "01" => Q1 <= '0';
36                 WHEN "10" => Q1 <= '1';
37                 WHEN OTHERS => Q1 <= NOT Q1;
38             END CASE;


```

```

39
40     CASE JK1 IS
41         WHEN "00" => Q2 <= Q2;
42         WHEN "01" => Q2 <= '0';
43         WHEN "10" => Q2 <= '1';
44         WHEN OTHERS => Q2 <= NOT Q2;
45     END CASE;
46
47     CASE JK2 IS
48         WHEN "00" => Q3 <= Q3;
49         WHEN "01" => Q3 <= '0';
50         WHEN "10" => Q3 <= '1';
51         WHEN OTHERS => Q3 <= NOT Q3;
52     END CASE;
53
54     CASE JK3 IS
55         WHEN "00" => Q4 <= Q4;
56         WHEN "01" => Q4 <= '0';
57         WHEN "10" => Q4 <= '1';
58         WHEN OTHERS => Q4 <= NOT Q4;
59     END CASE;
60
61     END IF;
62     END PROCESS;
63     Q <= Q4;
64 END BEHAV;


```

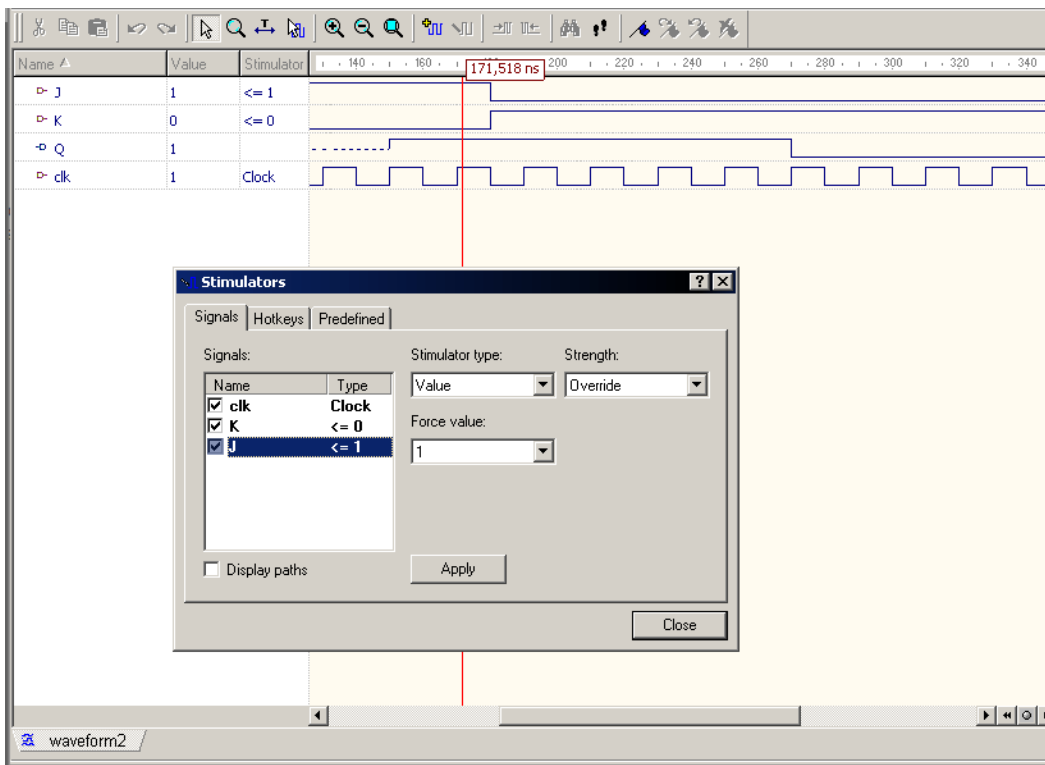WARP done.
 Compilation successful.
 genvhdl -s 1164_VHDL -i "PD.vhd"
 Running: batnova -v -f -lstd_logic PD
 genvhdl completed
 Done.



 0:38, viernes, 26 de marzo de 2021
 Simulation has been initialized
 Selected Top-Level: SP (BEHAV)
 KERNEL: stopped at time: 60 ns
 KERNEL: stopped at time: 120 ns
 KERNEL: stopped at time: 180 ns
 KERNEL: stopped at time: 280 ns
 KERNEL: stopped at time: 380 ns
 KERNEL: stopped at time: 480 ns

Entrada Serie - salida Paralelo (Con JK)
de 5 bits.



Enlace: <https://tinyurl.com/yzh73dag>

The screenshot shows the Quartus II software interface with the following components:

- Top Bar:** Displays the project name "P42 [Device - PALCE22Y10-25PC/P1] - Galaxy - [PD2.vhd]".
- Menu Bar:** Includes File, Edit, View, Format, Project, Compile, Templates, Bookmarks, Tools, Window, and Help.
- Toolbox:** Contains various icons for file operations, compilation, and simulation.
- Left Panel:** Shows the "Source Files - Project: P42" tree with files PD2.vhd, PD.vhd, P42.vhd, and Rom Files.
- Main Editor:** Displays the VHDL code for the counter circuit.

```

1  LIBRARY IEEE;
2  USE IEEE.STD_LOGIC_1164.ALL;
3
4  ENTITY SP IS
5      PORT (clk, J, K : in std_logic;
6            Q : OUT STD_LOGIC_VECTOR (4 downto 0));
7  END SP;
8
9  ARCHITECTURE BEHAV OF SP IS
10
11     SIGNAL JK, JKO, JK1, JK2, JK3: STD_LOGIC_VECTOR (1 downto 0);
12     SIGNAL Q_aux : STD_LOGIC_VECTOR (4 downto 0);
13
14 BEGIN
15     JK <= J&K;
16     JKO <= Q_aux(0) & (NOT Q_aux(0));
17     JK1 <= Q_aux(1) & (NOT Q_aux(1));
18     JK2 <= Q_aux(2) & (NOT Q_aux(2));
19     JK3 <= Q_aux(3) & (NOT Q_aux(3));
20
21     PROCESS (clk)
22     BEGIN
23         IF ((clk' EVENT) AND (clk = '1')) THEN
24             CASE JK IS
25                 WHEN "00" => Q_aux(0) <= Q_aux(0);
26                 WHEN "01" => Q_aux(0) <= '0';
27                 WHEN "10" => Q_aux(0) <= '1';
28                 WHEN OTHERS => Q_aux(0) <= NOT Q_aux(0);
29             END CASE;
30
31             CASE JKO IS
32                 WHEN "00" => Q_aux(1) <= Q_aux(1);
33                 WHEN "01" => Q_aux(1) <= '0';
34                 WHEN "10" => Q_aux(1) <= '1';
35                 WHEN OTHERS => Q_aux(1) <= NOT Q_aux(1);
36             END CASE;
37
38             CASE JK1 IS

```

```

39     WHEN "00" => Q_aux(2) <= Q_aux(2);
40     WHEN "01" => Q_aux(2) <= '0';
41     WHEN "10" => Q_aux(2) <= '1';
42     WHEN OTHERS => Q_aux(2) <= NOT Q_aux(2);
43 END CASE;
44
45 CASE JK2 IS
46     WHEN "00" => Q_aux(3) <= Q_aux(3);
47     WHEN "01" => Q_aux(3) <= '0';
48     WHEN "10" => Q_aux(3) <= '1';
49     WHEN OTHERS => Q_aux(3) <= NOT Q_aux(3);
50 END CASE;
51
52 CASE JK3 IS
53     WHEN "00" => Q_aux(4) <= Q_aux(4);
54     WHEN "01" => Q_aux(4) <= '0';
55     WHEN "10" => Q_aux(4) <= '1';
56     WHEN OTHERS => Q_aux(4) <= NOT Q_aux(4);
57 END CASE;
58
59 END IF;
60 END PROCESS;
61 Q <= Q_aux;
62 END BEHAV;

```

WARP done.
 Compilation successful.
 genvhdl -s 1164_VHDL -i "PD2.vhd"
 Running: batnova -v -f -lstd_logic PD2
 genvhdl completed
 Done.

